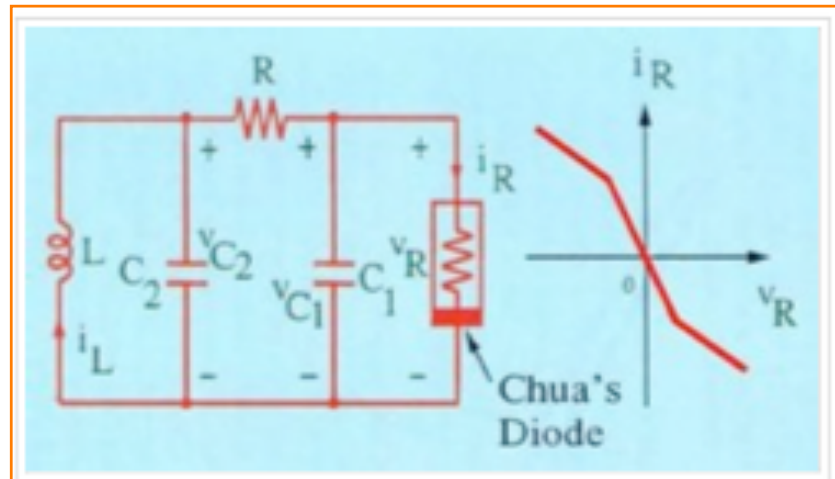


Hands_on session-F (Room # 404)
on
Dynamics of Nonlinear Electronic Circuits

Gautam Sethia and Mitesh Patel


Chua circuit




- RLC circuit
- Chua diode
- **PSPICE** simulation
- Build a circuit

One of the simplest nonlinear circuits that can demonstrate a host of nonlinear phenomena – such as limit cycle oscillations, period doubling sequence, chaos, scroll attractors etc.


Chua circuit output

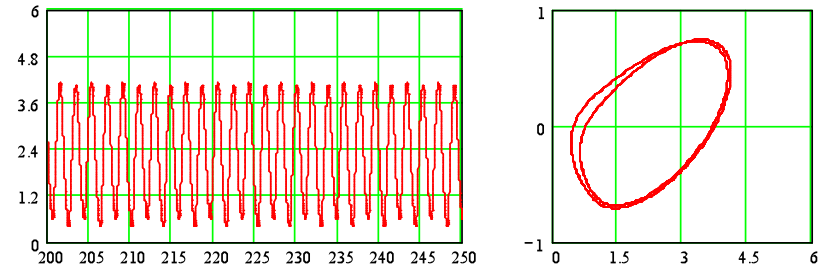


$R_1 = 1740 \Omega$

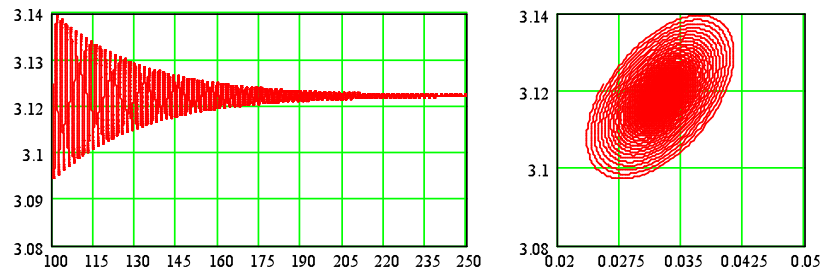


$R_1 = 1900 \Omega$

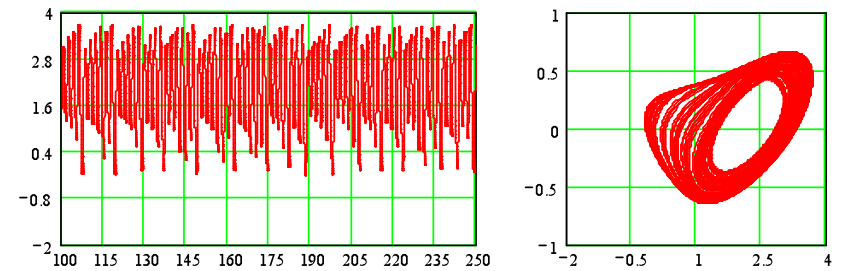

$R_1 = 1680 \Omega$

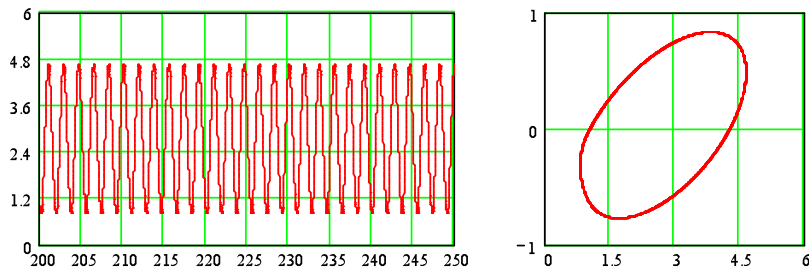




$R_1 = 1820 \Omega$

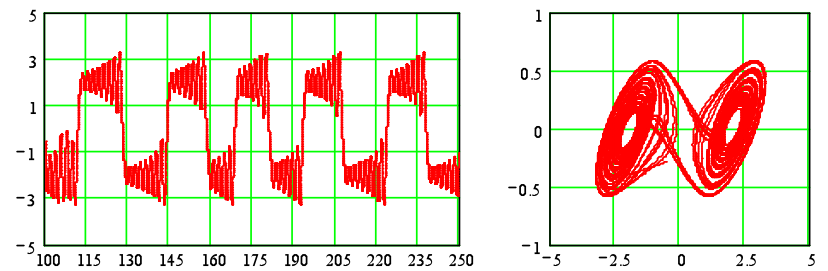

$R_1 = 1620 \Omega$

Coupled oscillators

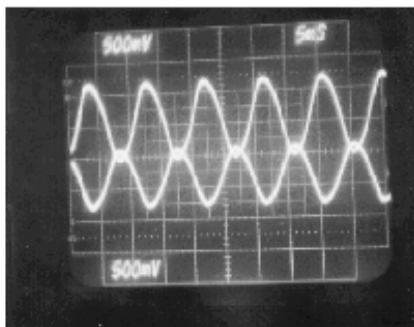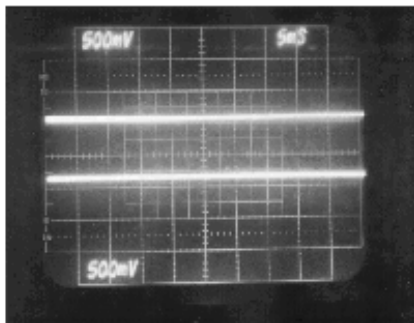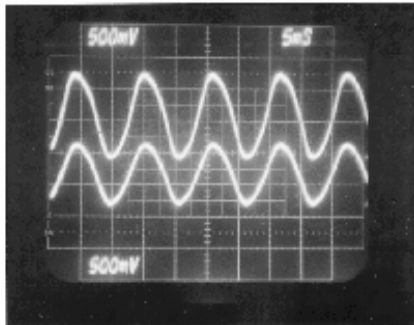- What happens when two oscillators are coupled to each other ?



Collective dynamics of many oscillators?

- *Synchrony*
- *Pattern formation*
- *Paradigm for many applications*